

Circuits and Circuit Elements

Additional Practice A

Givens

1. $R = 160 \text{ k}\Omega$

$R_1 = 2.0R$

$R_2 = 3.0R$

$R_3 = 7.5R$

Solutions

$$R_{eq} = R_1 + R_2 + R_3 = 2.0R + 3.0R + 7.5R = 12.5R$$

$$R_{eq} = (12.5)(160 \text{ k}\Omega) = \boxed{2.0 \times 10^3 \text{ k}\Omega}$$

2. $R = 5.0 \times 10^8 \Omega$

$R_1 = \frac{1}{3}R$

$R_2 = \frac{2}{7}R$

$R_3 = \frac{1}{5}R$

$$R_{eq} = R_1 + R_2 + R_3 = \frac{1}{3}R + \frac{2}{7}R + \frac{1}{5}R$$

$$R_{eq} = \frac{35 + 30 + 21}{105}R = \frac{86}{105}R = \frac{86}{105}(5.0 \times 10^8 \Omega) = \boxed{4.1 \times 10^8 \Omega}$$

3. $R_1 = 16 \text{ k}\Omega$

$R_2 = 22 \text{ k}\Omega$

$R_3 = 32 \text{ k}\Omega$

$R_{eq} = 82 \text{ k}\Omega$

$$R_4 = R_{eq} - R_1 - R_2 - R_3 = 82 \text{ k}\Omega - 16 \text{ k}\Omega - 22 \text{ k}\Omega - 32 \text{ k}\Omega = \boxed{12 \text{ k}\Omega}$$

4. $R_1 = 3.0 \text{ k}\Omega$

$R_2 = 4.0 \text{ k}\Omega$

$R_3 = 5.0 \text{ k}\Omega$

$P = (0.0100)(3.2 \text{ MW}) = 0.032 \text{ MW}$

$$R_{eq} = R_1 + R_2 + R_3 = 3.0 \text{ k}\Omega + 4.0 \text{ k}\Omega + 5.0 \text{ k}\Omega = 12.0 \text{ k}\Omega$$

$$P = \frac{(\Delta V)^2}{R}$$

$$\Delta V = \sqrt{PR_{eq}} = \sqrt{(3.2 \times 10^4 \text{ W})(1.20 \times 10^4 \Omega)} = \boxed{2.0 \times 10^4 \text{ V}}$$

5. $R_1 = 4.5 \Omega$

$R_2 = 4.0 \Omega$

$R_3 = 16.0 \Omega$

$$R_{12} = R_1 + R_2 = 4.5 \Omega + 4.0 \Omega = \boxed{8.5 \Omega}$$

$$R_{13} = R_1 + R_3 = 4.5 \Omega + 16.0 \Omega = \boxed{20.5 \Omega}$$

$$R_{23} = R_2 + R_3 = 4.0 \Omega + 16.0 \Omega = \boxed{20.0 \Omega}$$

6. $R_1 = 2.20 \times 10^2 \Omega$

$\Delta V_i = 1.20 \times 10^2 \text{ V}$

$\Delta V_f = 138 \text{ V}$

Because the current is unchanged, the following relationship can be written.

$$\frac{V_i}{R_1} = \frac{V_f}{R_1 + R_2}$$

$$R_2 = \frac{V_f R_1 - V_i R_1}{V_i} = \frac{(138 \text{ V})(220 \Omega) - (120 \text{ V})(220 \Omega)}{120 \text{ V}}$$

$$R_2 = \frac{30400 \text{ V} \cdot \Omega - 26400 \text{ V} \cdot \Omega}{120 \text{ V}} = \frac{4000 \text{ V} \cdot \Omega}{120 \text{ V}} = \boxed{33 \Omega}$$

Givens

$$\begin{aligned} 7. \quad R_1 &= 3.6 \times 10^{-5} \, \Omega \\ R_2 &= 8.4 \times 10^{-6} \, \Omega \\ I &= 280 \, \text{A} \end{aligned}$$

Solutions

$$\begin{aligned} R_{eq} &= R_1 + R_2 = 3.6 \times 10^{-5} \, \Omega + 8.4 \times 10^{-6} \, \Omega = 4.4 \times 10^{-5} \, \Omega \\ P &= I^2 R_{eq} = (280 \, \text{A})^2 (4.4 \times 10^{-5} \, \Omega) = \boxed{3.4 \, \text{W}} \end{aligned}$$

Additional Practice B

$$\begin{aligned} 1. \quad R_1 &= 1.8 \, \Omega \\ R_2 &= 5.0 \, \Omega \\ R_3 &= 32 \, \Omega \end{aligned}$$

$$\begin{aligned} R_{eq} &= \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = \left(\frac{1}{1.8 \, \Omega} + \frac{1}{5.0 \, \Omega} + \frac{1}{32 \, \Omega} \right)^{-1} \\ R_{eq} &= \left(0.55 \frac{1}{\Omega} + 0.20 \frac{1}{\Omega} + 0.031 \frac{1}{\Omega} \right)^{-1} = \left(0.78 \frac{1}{\Omega} \right)^{-1} = \boxed{1.3 \, \Omega} \end{aligned}$$

$$\begin{aligned} 2. \quad R &= 450 \, \Omega \\ R_1 &= R \\ R_2 &= 2.0R \\ R_3 &= 0.50R \end{aligned}$$

$$\begin{aligned} R_{eq} &= \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = \left(\frac{1}{450 \, \Omega} + \frac{1}{900 \, \Omega} + \frac{1}{220 \, \Omega} \right)^{-1} \\ R_{eq} &= \left(0.0022 \frac{1}{\Omega} + 0.0011 \frac{1}{\Omega} + 0.0045 \frac{1}{\Omega} \right)^{-1} = \left(0.0078 \frac{1}{\Omega} \right)^{-1} = \boxed{1.3 \times 10^2 \, \Omega} \end{aligned}$$

$$\begin{aligned} 3. \quad R_1 &= 2.48 \times 10^{-2} \, \Omega \\ R_{eq} &= 6.00 \times 10^{-3} \, \Omega \end{aligned}$$

$$\begin{aligned} R_2 &= \left(\frac{1}{R_{eq}} - \frac{1}{R_1} \right)^{-1} = \left(\frac{1}{6.00 \times 10^{-3} \, \Omega} - \frac{1}{2.48 \times 10^{-2} \, \Omega} \right)^{-1} \\ R_2 &= \left(167 \frac{1}{\Omega} - 80.6 \frac{1}{\Omega} \right)^{-1} = \left(86 \frac{1}{\Omega} \right)^{-1} = \boxed{0.012 \, \Omega} \end{aligned}$$

$$\begin{aligned} 4. \quad R_1 &= R \\ R_2 &= 3R \\ R_3 &= 7R \\ R_4 &= 11R \\ R_{eq} &= 6.38 \times 10^{-2} \, \Omega \end{aligned}$$

$$\begin{aligned} R_{eq} &= \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)^{-1} = \left(\frac{1}{R} + \frac{1}{3R} + \frac{1}{7R} + \frac{1}{11R} \right)^{-1} \\ R_{eq} &= \left(\frac{231 + 77 + 33 + 21}{231R} \right)^{-1} = \left(\frac{362}{231R} \right)^{-1} = \left(\frac{1.57}{R} \right)^{-1} \\ R &= 1.57 R_{eq} = 1.57 (6.38 \times 10^{-2} \, \Omega) = \boxed{0.100 \, \Omega} \end{aligned}$$

$$\begin{aligned} 5. \quad \text{ratio} &= 1.22 \times 10^{-2} \, \Omega/\text{m} \\ \ell &= 1813 \, \text{km} \end{aligned}$$

$$\begin{aligned} R_1 &= \frac{1}{2}R \\ R_2 &= \frac{1}{4}R \\ R_3 &= \frac{1}{5}R \\ R_4 &= \frac{1}{20}R \end{aligned}$$

$$\text{a. } R = (\text{ratio})(\ell) = (1.22 \times 10^{-2} \, \Omega/\text{m})(1.813 \times 10^6 \, \text{m}) = \boxed{2.21 \times 10^4 \, \Omega}$$

$$\begin{aligned} \text{b. } R_{eq} &= \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)^{-1} = \left(\frac{2}{R} + \frac{4}{R} + \frac{5}{R} + \frac{20}{R} \right)^{-1} \\ R_{eq} &= \left(\frac{31}{R} \right)^{-1} = \left(\frac{31}{1.00 \times 10^{10} \, \Omega} \right)^{-1} = \boxed{3.23 \times 10^8 \, \Omega} \end{aligned}$$

$$\begin{aligned} 6. \quad \Delta V &= 14.4 \, \text{V} \\ P &= 225 \, \text{W} \end{aligned}$$

$$\begin{aligned} P &= \frac{(\Delta V)^2}{R} \\ R &= \frac{(\Delta V)^2}{P} = \frac{(14.4 \, \text{V})^2}{225 \, \text{W}} = \boxed{0.922 \, \Omega} \\ R_{eq} &= \left(\frac{4}{R} \right)^{-1} = \frac{R}{4} = \frac{0.922 \, \Omega}{4} = 0.230 \, \Omega \\ I &= \frac{\Delta V}{R_{eq}} = \frac{14.4 \, \text{V}}{0.230 \, \Omega} = \boxed{62.6 \, \text{A}} \end{aligned}$$

Givens

$$\begin{aligned} 7. \quad L &= 3.22 \times 10^5 \text{ km} \\ \ell &= 1.00 \times 10^3 \text{ km} \\ \text{ratio} &= 1.0 \times 10^{-2} \Omega/\text{m} \\ \Delta V &= 1.50 \text{ V} \end{aligned}$$

Solutions

$$\begin{aligned} R_{eq} &= N \left(\frac{1}{R} \right) \quad \text{where } N = \frac{L}{\ell} \text{ and } R = (\text{ratio})\ell \\ R_{eq} &= \left[\frac{L}{(\text{ratio})\ell^2} \right]^{-1} = \left[\frac{3.22 \times 10^8 \text{ m}}{(1.0 \times 10^{-2} \Omega/\text{m})(1.00 \times 10^6 \text{ m})^2} \right]^{-1} = 31 \Omega \\ I &= \frac{\Delta V}{R_{eq}} = \frac{1.50 \text{ V}}{31 \Omega} = \boxed{0.048 \text{ A}} \end{aligned}$$

Additional Practice C

$$\begin{aligned} 1. \quad R_1 &= 6.60 \times 10^2 \Omega \\ R_2 &= 2.40 \times 10^2 \Omega \\ R_3 &= 2.00 \times 10^2 \Omega \\ R_4 &= 2.00 \times 10^2 \Omega \end{aligned}$$

$$\begin{aligned} R_{12} &= R_1 + R_2 = 660 \Omega + 240 \Omega = 900 \Omega \\ R_{123} &= \left(\frac{1}{R_{12}} + \frac{1}{R_3} \right)^{-1} = \left(\frac{1}{900 \Omega} + \frac{1}{200 \Omega} \right)^{-1} \\ R_{123} &= \left(0.00111 \frac{1}{\Omega} + 0.00500 \frac{1}{\Omega} \right)^{-1} = \left(0.00611 \frac{1}{\Omega} \right)^{-1} = 164 \Omega \\ R_{eq} &= R_{123} + R_4 = 164 \Omega + 200 \Omega = \boxed{364 \Omega} \end{aligned}$$

$$\begin{aligned} 2. \quad \Delta V &= 24 \text{ V} \\ R_1 &= 2.0 \Omega \\ R_2 &= 4.0 \Omega \\ R_3 &= 6.0 \Omega \\ R_4 &= 3.0 \Omega \end{aligned}$$

$$\begin{aligned} R_{12} &= R_1 + R_2 = 2.0 \Omega + 4.0 \Omega = 6.0 \Omega \\ R_{34} &= \left(\frac{1}{R_3} + \frac{1}{R_4} \right)^{-1} = \left(\frac{1}{6.0 \Omega} + \frac{1}{3.0 \Omega} \right)^{-1} \\ R_{34} &= \left(0.17 \frac{1}{\Omega} + 0.33 \frac{1}{\Omega} \right)^{-1} = \left(0.50 \frac{1}{\Omega} \right)^{-1} = 2.0 \Omega \\ R_{eq} &= \left(\frac{1}{R_{12}} + \frac{1}{R_{34}} \right)^{-1} = \left(\frac{1}{6.0 \Omega} + \frac{1}{2.0 \Omega} \right)^{-1} \\ R_{eq} &= \left(0.17 \frac{1}{\Omega} + 0.50 \frac{1}{\Omega} \right)^{-1} = \left(0.67 \frac{1}{\Omega} \right)^{-1} = 1.5 \Omega \\ I &= \frac{\Delta V}{R_{eq}} = \frac{24 \text{ V}}{1.5 \Omega} = \boxed{16 \text{ A}} \end{aligned}$$

$$\begin{aligned} 3. \quad R_1 &= 2.5 \Omega \\ R_2 &= 3.5 \Omega \\ R_3 &= 3.0 \Omega \\ R_4 &= 4.0 \Omega \\ R_5 &= 1.0 \Omega \\ \Delta V &= 12 \text{ V} \end{aligned}$$

$$\begin{aligned} R_{12} &= R_1 + R_2 = 2.5 \Omega + 3.5 \Omega = 6.0 \Omega \\ R_{123} &= \left(\frac{1}{R_{12}} + \frac{1}{R_3} \right)^{-1} = \left(\frac{1}{6.0 \Omega} + \frac{1}{3.0 \Omega} \right)^{-1} \\ R_{123} &= \left(0.17 \frac{1}{\Omega} + 0.33 \frac{1}{\Omega} \right)^{-1} = \left(0.50 \frac{1}{\Omega} \right)^{-1} = 2.0 \Omega \\ R_{45} &= \left(\frac{1}{R_4} + \frac{1}{R_5} \right)^{-1} = \left(\frac{1}{4.0 \Omega} + \frac{1}{1.0 \Omega} \right)^{-1} \\ R_{45} &= \left(0.25 \frac{1}{\Omega} + 1.0 \frac{1}{\Omega} \right)^{-1} = \left(1.2 \frac{1}{\Omega} \right)^{-1} = 0.83 \Omega \\ R_{eq} &= R_{123} + R_{45} = 2.0 \Omega + 0.83 \Omega = \boxed{2.8 \Omega} \\ I &= \frac{\Delta V}{R} = \frac{12 \text{ V}}{2.8 \Omega} = \boxed{4.3 \text{ A}} \end{aligned}$$

4. $\Delta V = 1.00 \times 10^3 \text{ V}$

$R_1 = 1.5 \, \Omega$

$R_2 = 3.0 \, \Omega$

$R_3 = 1.0 \, \Omega$

$$R_{12} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \left(\frac{1}{1.5 \, \Omega} + \frac{1}{3.0 \, \Omega} \right)^{-1}$$

$$R_{12} = \left(0.67 \frac{1}{\Omega} + 0.33 \frac{1}{\Omega} \right)^{-1} = \left(1.00 \frac{1}{\Omega} \right)^{-1} = 1.00 \, \Omega$$

$$R_{eq} = R_{12} + R_3 = 1.00 \, \Omega + 1.0 \, \Omega = \boxed{2.0 \, \Omega}$$

$$P = \frac{(\Delta V)^2}{R_{eq}} = \frac{(1.00 \times 10^3 \text{ V})^2}{2.0 \, \Omega} = \boxed{5.0 \times 10^5 \text{ W}}$$

5. $\Delta V = 2.00 \times 10^3 \text{ V}$

$I = 1.0 \times 10^{-8} \text{ A}$

$R_1 = r$

$R_2 = 3r$

$R_3 = 2r$

$R_4 = 4r$

$$R_{eq} = \frac{\Delta V}{I} = \frac{2.00 \times 10^3 \text{ V}}{1.0 \times 10^{-8} \text{ A}} = \boxed{2.0 \times 10^{11} \, \Omega}$$

$$R_{12} = R_1 + R_2 = r + 3r = 4r$$

$$R_{34} = R_3 + R_4 = 2r + 4r = 6r$$

$$R_{eq} = \left(\frac{1}{R_{12}} + \frac{1}{R_{34}} \right)^{-1} = \left(\frac{1}{4r} + \frac{1}{6r} \right)^{-1}$$

$$R_{eq} = \left(\frac{3+2}{12r} \right)^{-1} = \left(\frac{5}{12r} \right)^{-1} = \frac{12}{5} r$$

$$r = \frac{5}{12} R_{eq} = \frac{5}{12} (2.0 \times 10^{11} \, \Omega) = \boxed{8.3 \times 10^{10} \, \Omega}$$

6. $P = 6.0 \times 10^5 \text{ W}$

$\Delta V = 220 \text{ V}$

$$R = \frac{(\Delta V)^2}{P} = \frac{(220 \text{ V})^2}{6.0 \times 10^5 \text{ W}} = \boxed{8.1 \times 10^{-2} \, \Omega}$$

$$R_{12} = R_{45} = 2R = 2(0.081 \, \Omega) = 0.16 \, \Omega$$

$$R_{12345} = \left(\frac{1}{R_{12}} + \frac{1}{R_3} + \frac{1}{R_{45}} \right)^{-1} = \left(\frac{1}{0.16 \, \Omega} + \frac{1}{0.081 \, \Omega} + \frac{1}{0.16 \, \Omega} \right)^{-1}$$

$$R_{12345} = \left(6.2 \frac{1}{\Omega} + 12 \frac{1}{\Omega} + 6.2 \frac{1}{\Omega} \right)^{-1} = \left(24 \frac{1}{\Omega} \right)^{-1} = 0.042 \, \Omega$$

$$R_{eq} = R_{12345} + R_6 = 0.042 \, \Omega + 0.081 \, \Omega = 0.123 \, \Omega$$

$$P = \frac{(\Delta V)^2}{R_{eq}} = \frac{(220 \text{ V})^2}{0.123 \, \Omega} = \boxed{3.9 \times 10^5 \text{ W}}$$

Additional Practice D

1. $R = 8.1 \times 10^{-2} \, \Omega$

$R_{eq} = 0.123 \, \Omega$

$\Delta V = 220 \text{ V}$

$R_{12} = R_{45} = 0.16 \, \Omega$

$R_{12345} = 0.042 \, \Omega$

a. $I = \frac{\Delta V}{R_{eq}} = \frac{220 \text{ V}}{0.123 \, \Omega} = 1800 \text{ A}$

$$\Delta V_{12345} = IR_{12345} = (1800 \text{ A})(0.042 \, \Omega) = 76 \text{ V}$$

$$\Delta V_3 = \Delta V_{12345} = \boxed{76 \text{ V}}$$

$$I_3 = \frac{\Delta V_3}{R_3} = \frac{76 \text{ V}}{8.1 \times 10^{-2} \, \Omega} = \boxed{9.4 \times 10^2 \text{ A}}$$

Givens

Solutions

b. $\Delta V_{12} = \Delta V_{12345} = 76 \text{ V}$

$$I_{12} = \frac{\Delta V_{12}}{R_{12}} = \frac{76 \text{ V}}{0.16 \Omega} = 4.8 \times 10^2 \text{ A}$$

$$I_2 = I_{12} = \boxed{4.8 \times 10^2 \text{ A}}$$

$$\Delta V_2 = I_2 R_2 = (4.8 \times 10^2 \text{ A})(8.1 \times 10^{-2} \Omega) = \boxed{39 \text{ V}}$$

c. Same as part b:

$$I_4 = \boxed{4.8 \times 10^2 \text{ A}}$$

$$\Delta V_4 = \boxed{39 \text{ V}}$$

2. $\Delta V = 12 \text{ V}$

$$R_1 = 2.5 \Omega$$

$$R_3 = 3.0 \Omega$$

$$R_4 = 4.0 \Omega$$

$$R_5 = 1.0 \Omega$$

$$R_{12} = 6.0 \Omega$$

$$R_{123} = 2.0 \Omega$$

$$R_{45} = 0.83 \Omega$$

$$R_{eq} = 2.8 \Omega$$

$$I = 4.3 \text{ A}$$

a. $\Delta V_{45} = IR_{45} = (4.3 \text{ A})(0.83 \Omega) = 3.6 \text{ V}$

$$\Delta V_5 = \Delta V_{45} = \boxed{3.6 \text{ V}}$$

$$I_5 = \frac{\Delta V_5}{R_5} = \frac{3.6 \text{ V}}{1.0 \Omega} = \boxed{3.6 \text{ A}}$$

b. $\Delta V_{123} = IR_{123} = (4.3 \text{ A})(2.0 \Omega) = 8.6 \text{ V}$

$$\Delta V_{12} = \Delta V_{123} = 8.6 \text{ V}$$

$$I_1 = I_{12} = \frac{\Delta V_{12}}{R_{12}} = \frac{8.6 \text{ V}}{6.0 \Omega} = \boxed{1.4 \text{ A}}$$

$$\Delta V_1 = I_1 R_1 = (1.4 \text{ A})(2.5 \Omega) = \boxed{3.5 \text{ V}}$$

c. $I_{45} = I = 4.3 \text{ A}$

$$\Delta V_{45} = I_{45} R_{45} = (4.3 \text{ A})(0.83 \Omega) = 3.6 \text{ V}$$

$$V_4 = \Delta V_{45} = \boxed{3.6 \text{ V}}$$

$$I_4 = \frac{\Delta V_4}{R_4} = \frac{3.6 \text{ V}}{4.0 \Omega} = \boxed{0.90 \text{ A}}$$

d. $\Delta V_3 = \Delta V_{123} = \boxed{8.6 \text{ V}}$

$$I_3 = \frac{\Delta V_3}{R_3} = \frac{8.6 \text{ V}}{3.0 \Omega} = \boxed{2.9 \text{ A}}$$

Givens

- 3.** $R_1 = 15\ \Omega$
 $R_2 = 3.0\ \Omega$
 $R_3 = 2.0\ \Omega$
 $R_4 = 5.0\ \Omega$
 $R_5 = 7.0\ \Omega$
 $R_6 = 3.0\ \Omega$
 $R_7 = 3.0 \times 10^1\ \Omega$
 $\Delta V = 2.00 \times 10^3\ \text{V}$

Solutions

$$\begin{aligned}
 R_{23} &= R_2 + R_3 = 3.0\ \Omega + 2.0\ \Omega = 5.0\ \Omega \\
 R_{234} &= \left(\frac{1}{R_{23}} + \frac{1}{R_4} \right)^{-1} = \left(\frac{1}{5.0\ \Omega} + \frac{1}{5.0\ \Omega} \right)^{-1} \\
 R_{234} &= \left(0.40 \frac{1}{\Omega} \right)^{-1} = 2.5\ \Omega \\
 R_{56} &= R_5 + R_6 = 7.0\ \Omega + 3.0\ \Omega = 10.0\ \Omega \\
 R_{567} &= \left(\frac{1}{R_{56}} + \frac{1}{R_7} \right)^{-1} = \left(\frac{1}{10.0\ \Omega} + \frac{1}{30\ \Omega} \right)^{-1} \\
 R_{567} &= \left(0.100 \frac{1}{\Omega} + 0.033 \frac{1}{\Omega} \right)^{-1} = \left(0.133 \frac{1}{\Omega} \right)^{-1} = 7.52\ \Omega \\
 R_{eq} &= R_1 + R_{234} + R_{567} = 15\ \Omega + 2.5\ \Omega + 7.52\ \Omega = 25\ \Omega
 \end{aligned}$$

a. $I = \frac{\Delta V}{R_{eq}} = \frac{2.00 \times 10^3\ \text{V}}{25\ \Omega} = 80\ \text{A}$

$$\Delta V_{234} = IR_{234} = (80\ \text{A})(2.5\ \Omega) = 2.0 \times 10^2\ \text{V}$$

$$\Delta V_4 = \Delta V_{234} = \boxed{2.0 \times 10^2\ \text{V}}$$

$$I_4 = \frac{\Delta V_4}{R_4} = \frac{200\ \text{V}}{5.0\ \Omega} = \boxed{4.0 \times 10^1\ \text{A}}$$

b. $\Delta V_{23} = \Delta V_{234} = 200\ \text{V}$

$$I_{23} = \frac{\Delta V_{23}}{R_{23}} = \frac{200\ \text{V}}{5.0\ \Omega} = 40\ \text{A}$$

$$I_3 = I_{23} = \boxed{4.0 \times 10^1\ \text{A}}$$

$$\Delta V_3 = I_3 R_3 = (40\ \text{A})(2.0\ \Omega) = \boxed{8.0 \times 10^1\ \text{V}}$$

c. $I_{567} = I = 80\ \text{A}$

$$V_{567} = I_{567} R_{567} = (80\ \text{A})(7.52\ \Omega) = 600\ \text{V}$$

$$\Delta V_{56} = \Delta V_{567} = 600\ \text{V}$$

$$I_{56} = \frac{\Delta V_{56}}{R_{56}} = \frac{600\ \text{V}}{10.0\ \Omega} = 60\ \text{A}$$

$$I_5 = I_{56} = \boxed{6.0 \times 10^1\ \text{A}}$$

$$\Delta V_5 = I_5 R_5 = (60\ \text{A})(7.0\ \Omega) = \boxed{4.2 \times 10^2\ \text{V}}$$

d. $\Delta V_7 = \Delta V_{567} = \boxed{6.0 \times 10^2\ \text{V}}$

$$I_7 = \frac{\Delta V_7}{R_7} = \frac{600\ \text{V}}{30\ \Omega} = \boxed{2.0 \times 10^1\ \text{A}}$$